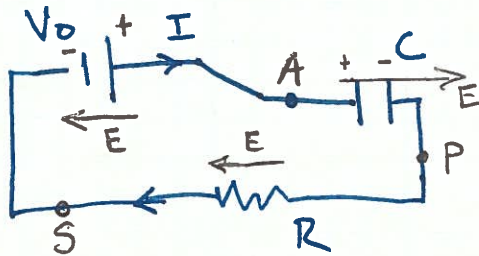


## RC Circuits



$$V_C = V_A - V_P$$


$$V_R = V_P - V_S = IR$$

Capacitor

at  $t=0$  no charge on capacitor,  $V_C = 0$

at  $t>0$ ,  $V_C \uparrow$ ,  $I \downarrow$

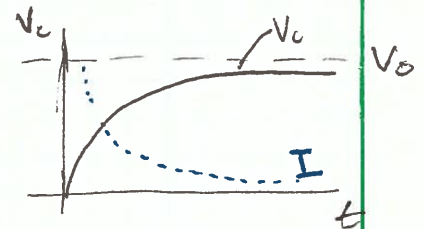as  $t \rightarrow \infty$ , cap is fully charged  $V_C \rightarrow V_0$ ,  $I = 0$



Now,  $\oint \vec{E} \cdot d\vec{l} = 0$  (was not true w/ inductor)

Kirchoff:

$$+V_C + IR - V_0 = 0$$

$$I = \frac{dQ}{dt}$$

$$V_C = Q/C$$

$$\boxed{\frac{Q}{C} + \frac{dQ}{dt}R - V_0 = 0}$$

$$\text{Sol'n: } Q = V_0 C (1 - e^{-t/RC})$$


$$I = \frac{V_0}{R} e^{-t/RC}$$

$$V_C = \frac{Q}{C} = V_0 (1 - e^{-t/RC})$$

Table:


$t$	$I$	$V_C$	$R$	$C$	$RC$
0	$V_0/R$	0	1Ω	1μF	1ms
$\infty$	0	$V_0$	100mΩ	1μF	10·kS
RC	$\frac{1}{e} \frac{V_0}{R}$	$(1 - \frac{1}{e})V_0$			

Add to previous circuit...

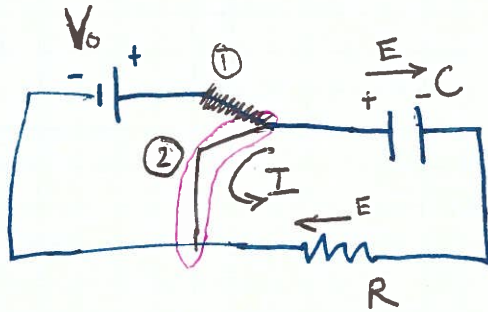

Capacitor is charged, now short power supply, now capacitor is discharging and resistor dissipates energy as heat ( $I^2R$  ... power)


We can modify our figure

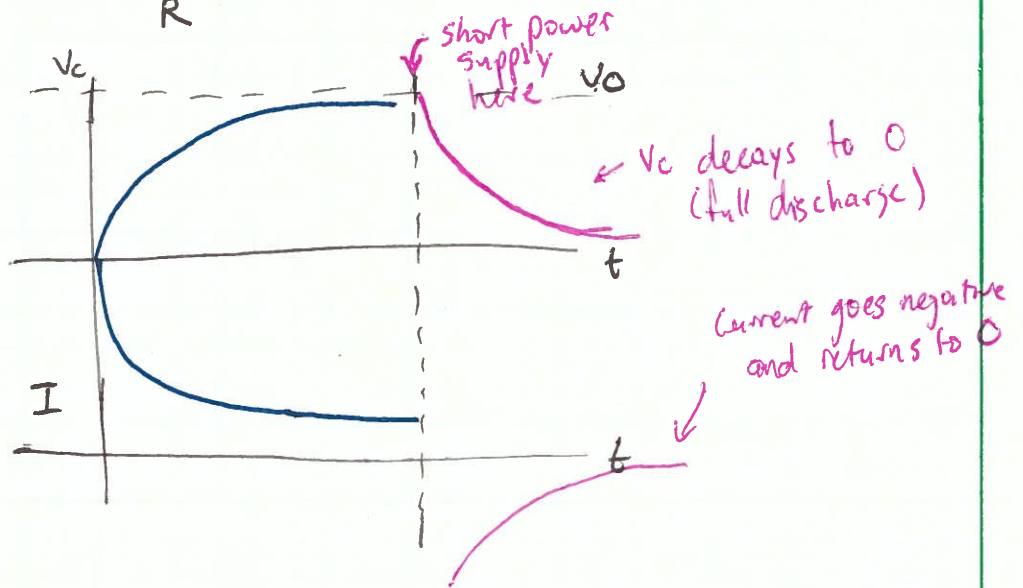

DEMO


Flip switch from position 1 (charge capacitor) to position 2 (discharge capacitor, short power supply).  $V_0 = 1V$ ,  $R = 6k\Omega$ ,  $C = 1\mu F$

So  $RC = 6 \times 10^{-4} s = .6 ms$

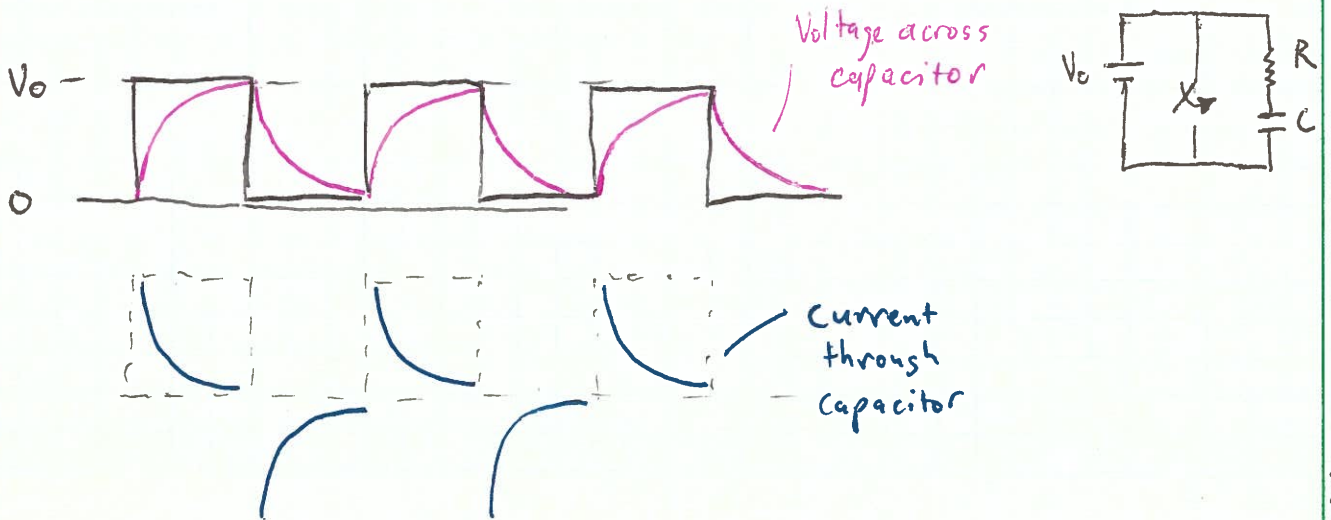

# TRANSFORMERS

ALWAYS AC

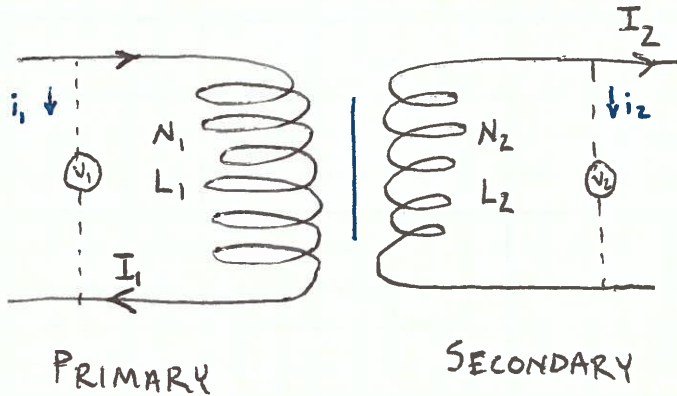

FARADAY  $\oint \mathbf{E} \cdot d\mathbf{l} = -\frac{d}{dt} \Phi_B$

$$0 - V_1 = -L_1 \frac{dI_1}{dt} = \mathcal{E}_1 = -N_1 \frac{d\phi_1}{dt}$$

$$0 + V_2 = -L_2 \frac{dI_2}{dt} = \mathcal{E}_2 = -N_2 \frac{d\phi_2}{dt}$$


$$\left| \frac{V_2}{V_1} \right| = \frac{N_2}{N_1}$$

## DEMO Transformer

$$N_1 = 220 \quad N_2 = 1$$

$$V_1 = 110 \text{ V}, \quad f = 60 \text{ Hz}$$
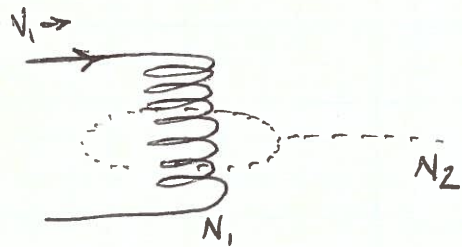
$$\hookrightarrow \underline{V_1 = 110\sqrt{2} \cos(120\pi t)}$$




W/ N<sub>2</sub> = 1 we expect  $V_2 = \sim \frac{110 \text{ V}}{220} = \underline{.5 \text{ V}}$

N<sub>2</sub> = 4 we expect  $V_2 = \frac{4}{220} \cdot 110 \approx \underline{2 \text{ V}}$

## DEMO Transformer w/ huge secondary current

$$\left| \frac{I_2}{I_1} \right| = \frac{N_1}{N_2}$$

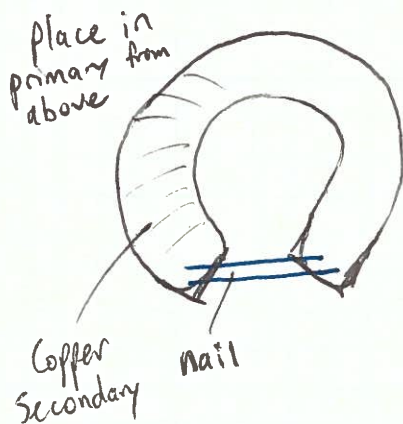

$$L_2 = 5 \times 10^{-7} \text{ H}$$

$$R_2 = 4 \times 10^{-4} \Omega$$

$$I_1 = 20 \text{ A}$$


↓ ?

$$I_2 = 220 \times 20 = 4400 \text{ A?}$$

(probably not...  $WL \approx R$ )

A lot of power through nail,  
it will glow red hot!

# DEMO: Spark Plugs in Cars

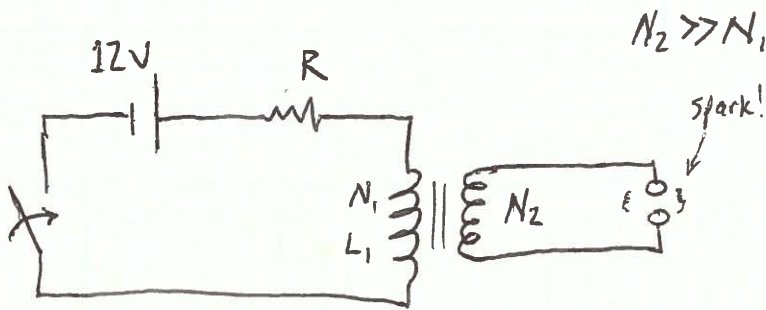

Time Constant:  $\frac{L}{R}$

1. Close switch, build up current in loop
2. Open switch, current drops ~~immediately~~ <sup>quickly</sup> at  $L/R_{new}$   
 $R_{new} \approx \infty$  (open)

So...

$$\frac{dI_1}{dt} \rightarrow \mathcal{E}_{ind1} \quad \frac{d\Phi_B}{dt} \left( \begin{array}{l} \text{huge change in magnetic} \\ \text{flux couples to current} \end{array} \right)$$

(really big when switch opened)      (huge EMF)

$$\mathcal{E}_{ind2} = \frac{N_2}{N_1} \mathcal{E}_{ind1} \quad (\mathcal{E}_{ind2} \text{ can be really big!})$$